

EE 40 MT1 *Handwritten notes*

$P = (R \cdot I) \cdot I = I^2 R$
 $P = \frac{dw}{dt} = \frac{dw}{dq} \frac{dq}{dt} = VI$
 $IW = IA \times IV$
 $e^- = 1.6 \times 10^{-19} C$



$E = qV_{AB}$ - Voltage difference
 ↳ Sdq or $q(t)$
 branch - sub element
 node - connection point
 extraordinary node - connection between branches
 loop - closed path

Resistor - affect voltage not current

$V = IR$
 $K = \frac{l}{\sigma A} = \rho \frac{l}{A}$ $l = \text{length}$
 $\sigma = \text{conductivity}$
 $A = \text{Area}$
 $\rho = \text{resistivity}$
 Thermistor - Resistance temp
 Piezoresistor - R sensitive to pressure

KCL: sum of currents entering node = 0 / closed boundary
 KVL: sum of voltages around closed path = 0

Source transformation

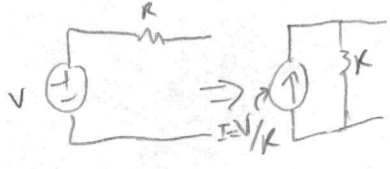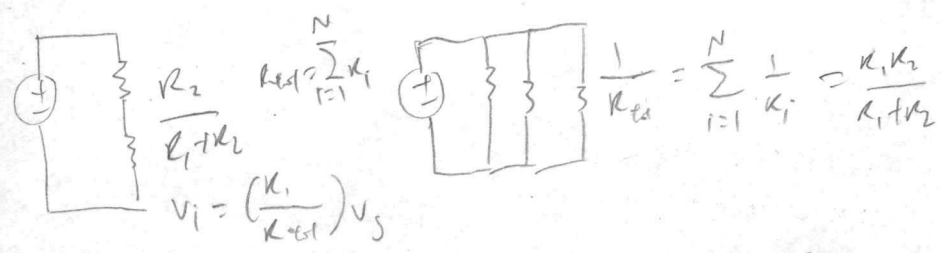

Y-Δ



$\Delta \rightarrow Y$ $Y \rightarrow \Delta$
 $R_1 = \frac{R_a R_b}{R_a + R_b + R_c}$ $R_a = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$
 $R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$ $R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$
 $R_3 = \frac{R_b R_c}{R_a + R_b + R_c}$ $R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$

for wheatstone bridge - if pos output, $V=0$ + resist.



Node/Voltage Apply KCL

Ignore all voltage sources & extraordinary nodes - treat as loads

Mesh/Current Apply KVL

Supernode: 2 meshes have current source in common - write equation for large loop, then write KVL w/ current.


Thevenin

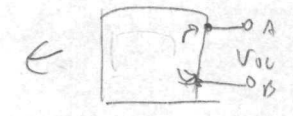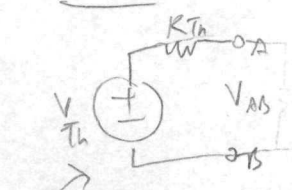

don't matter if resist. between A and B

$V_{oc} = V_{AB} = V_A - V_B$
 $V_B = \text{ground} = 0$

Norton

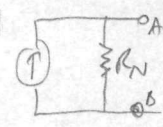

$R_{Th} = R_N$
 $I_N = \frac{V_{Th}}{R_{Th}}$

1) open/short circuit
↳ V_{Th} ↳ I / R

2) w/ short → short
(current → open)

* No dependent sources!

3) add external voltage source + solve for I