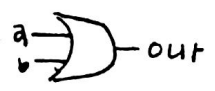


GATES


AND






OR





NOT

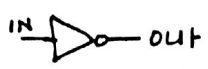


XOR

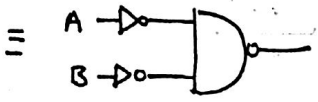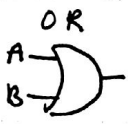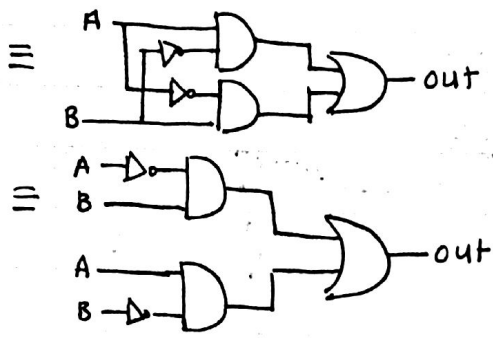

MUX

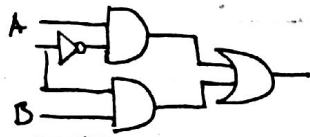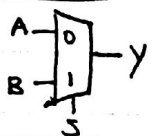

Decoder

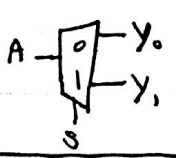

S	Y0	Y1
0	1	0
1	0	1

Static power


$$\sim \frac{V_{DD}^2}{R_{off}}$$

Switching Power

$$T = R_{on} \cdot C_{in}$$

⇒ max clock freq


Dynamic Power

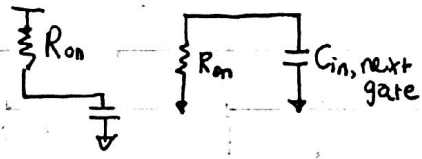

Half adder

- adds 2-bits


a	b	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

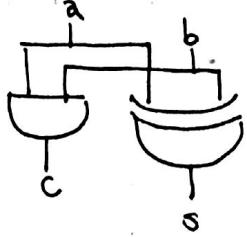

Full adder

- adds 3 bits

a	b	c	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

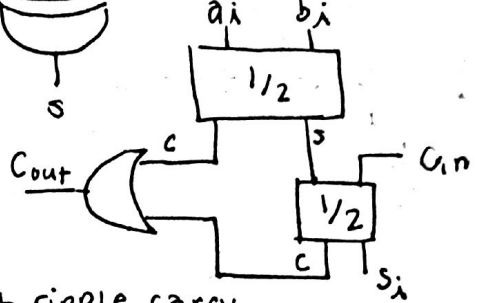

n-bit ripple carry

worst case delay: n * stage delay
 ↳ time b/w input came + output shows up

$$Q_{charge} = C_{in} \cdot V_{DD}$$


$$\Delta E_{battery} = Q \cdot V_{DD} = C_{in} \cdot V_{DD}^2$$

$$E_{cap} = \frac{1}{2} C_{in} V_{DD}^2$$


$$P_{avg} = \frac{\Delta E}{T_{avg, 0 \rightarrow 1}} = \frac{C_{in} \cdot V_{DD}^2}{T_{avg, 0 \rightarrow 1}}$$

$$= (f_{0 \rightarrow 1}) (C_{in}) (V_{DD}^2)$$


NMOS inverter (1N1)

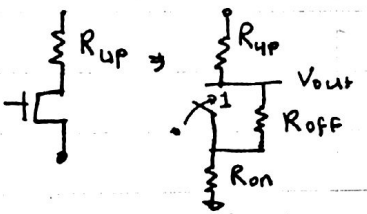

PMOS: 1N1P

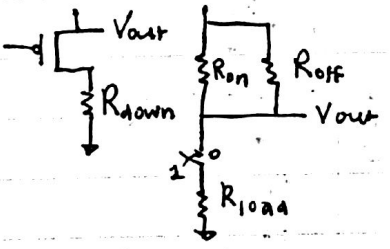

CMOS: 1N1C


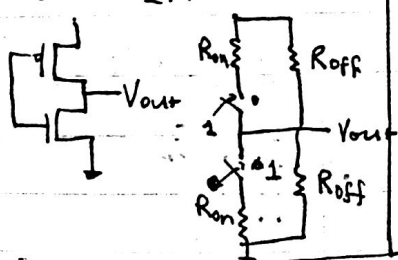


Edge-triggered D-flip



MxN register file

D-flip w/ enable

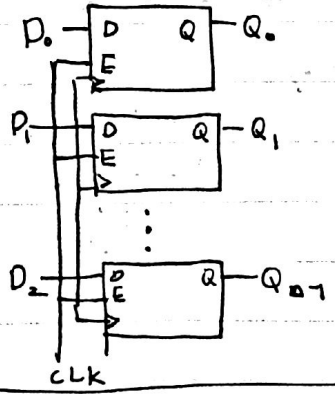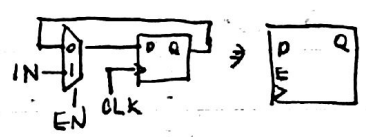




sampling

$$f_{min} = 2 \cdot \text{freq of signal} = f_{nyquist}$$

$$f_{nyquist} = \frac{f_{sample}}{2}$$

$$W_p = 2\pi \cdot f_{nyquist} = \frac{1}{R \cdot n \cdot C}$$
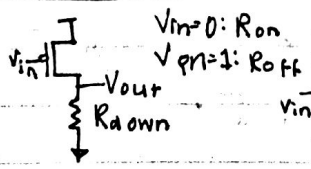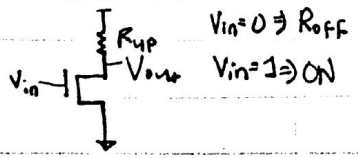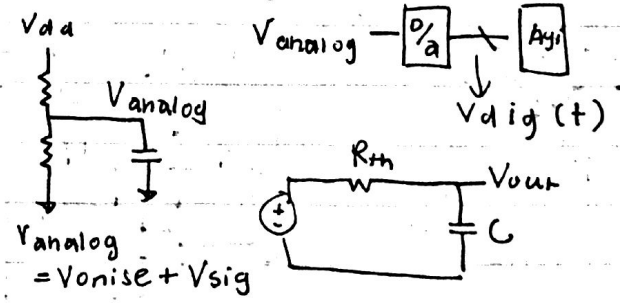
$$t_s = n \cdot T_s = n \cdot \frac{1}{f_s}$$




$V_{in}=0: R_{on}$ ON TOP
 R_{off} ON BOTTOM
 $V_{in}=1: R_{on}$ ON BOTTOM
 R_{off} ON TOP

HW 8


Representing Bits

$2^{10} \approx (10^3) \rightarrow 10 \text{ bits}$
 $10^6 \rightarrow (10^3)^2 \rightarrow (2^{10})^2 \rightarrow 20 \text{ bits}$
 $10^9 \rightarrow (10^3)^3 \rightarrow (2^{10})^3 \rightarrow 30 \text{ bits}$
 $3600 \rightarrow 2^2 \cdot 10^3 \rightarrow 12 \text{ bits}$

Finite state Machine

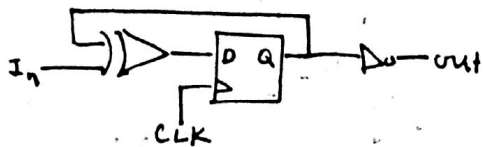


Artificial GATE

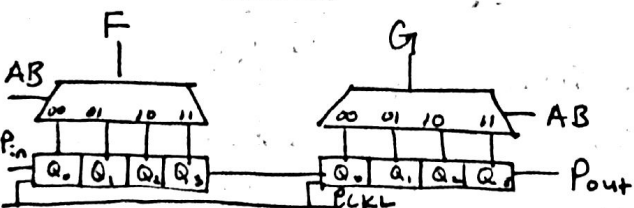


FPGA: Reconfigurable GATE


2^{2^n} functions

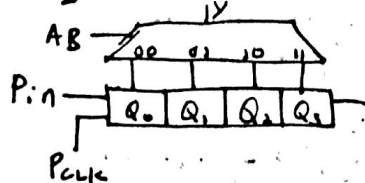


Dynamic Random Access Mem (DRAM)

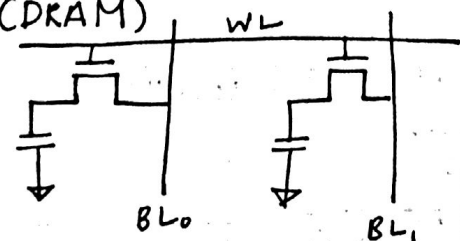


Static RAM

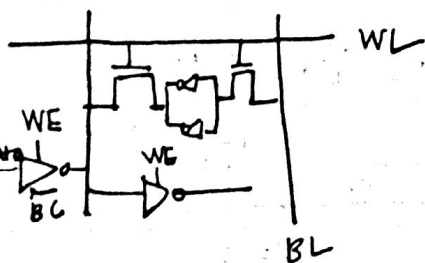


NOR

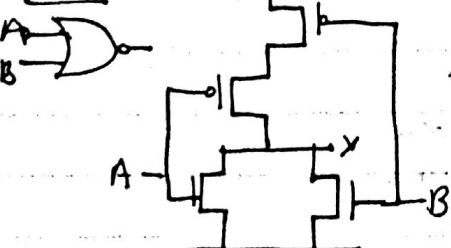


D-ff w/Enable

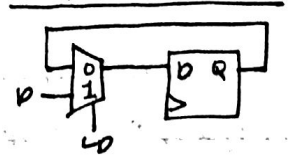


NAND

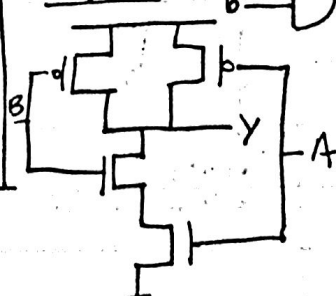


XOR

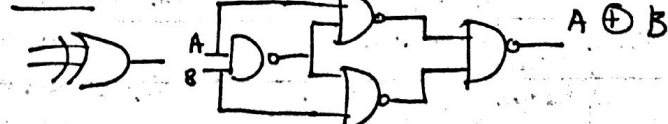


Enabled Inverters

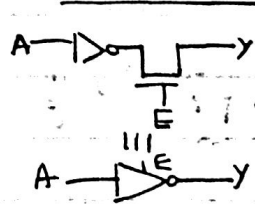



Inverter

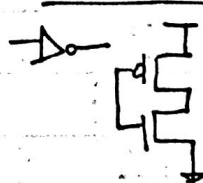



D-latch

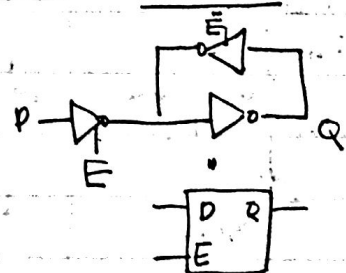

1 block (HW x 11)

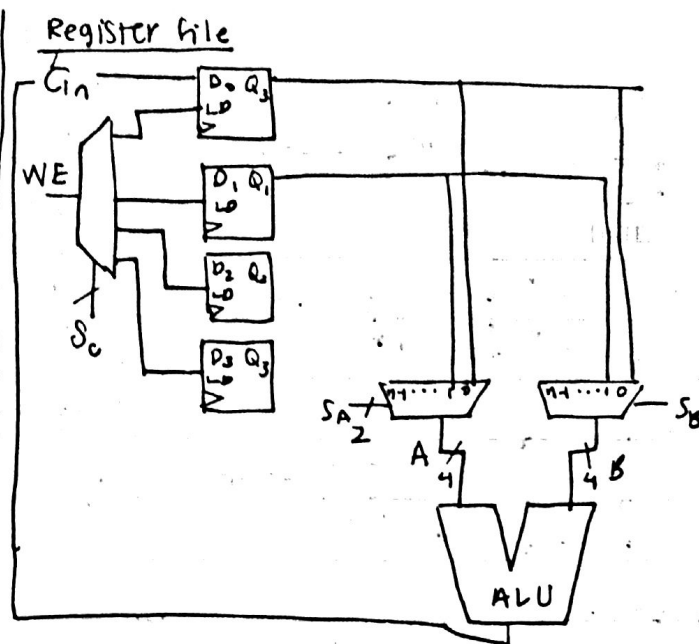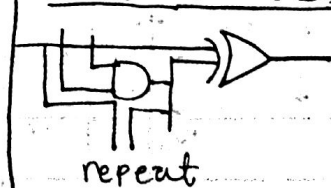


Shift register

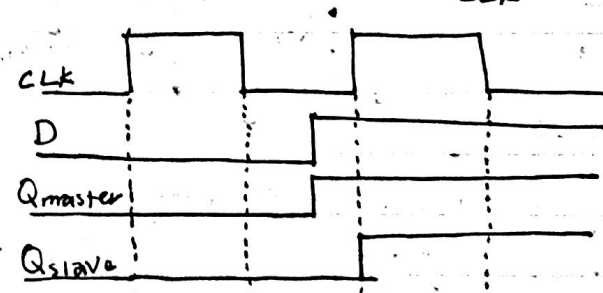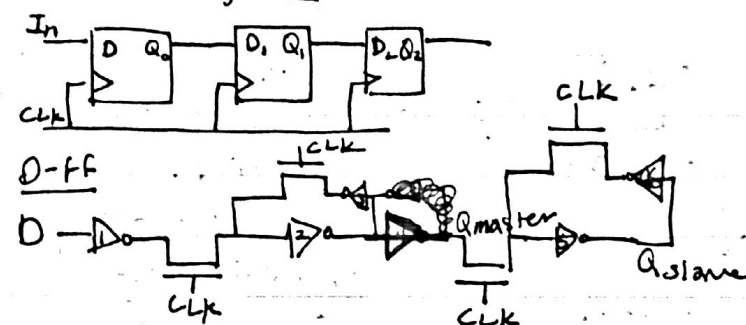

OP-AMPS


Ideal: $i_n = i_p = 0$
 $R_i = \infty, A = \infty, R_o = 0$
 $V_o = A(V_+ - V_-) = 10^6$

Non-inverting

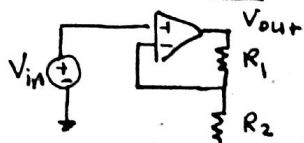


$$\frac{V_{out}}{V_{in}} = \frac{R_1 + R_2}{R_2} = 1 + \frac{R_1}{R_2}$$

Inverting

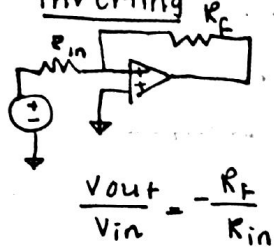


$$\frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}$$

Subtractor

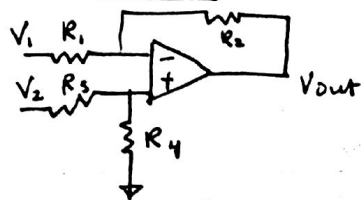


$$V_{out} = -V_1 \frac{R_2}{R_1} + \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) V_2$$

Summing

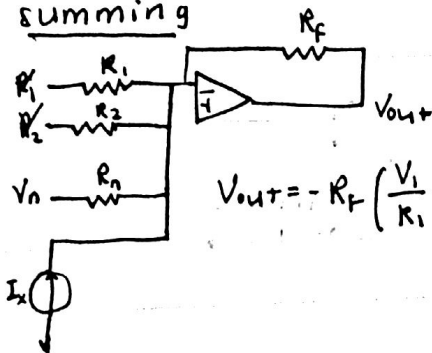

$$V_{out} = -R_f \left(\frac{V_1}{R_1} + \dots + \frac{V_n}{R_n} \right) + I_x$$


Integrator

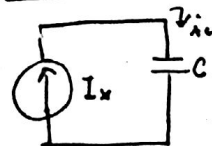

$$i_o = C \frac{dV_o}{dt} = i_x$$

$$\frac{dV_o}{dt} = \frac{1}{C} i_x$$

Inverting w/ capacitor

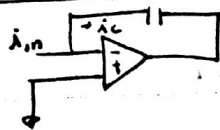


$$i_c = i_x$$

$$V_o(t) = -\int_0^t i_x dt$$

$$V_o = -V_o - \frac{1}{C} \int_0^t i_x dt$$

Differentiator

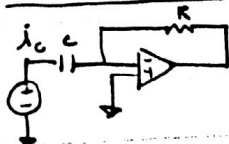

$$KVL: V_o = V_i$$

$$i_c = \frac{0 - V_o}{R}$$

APPROXIMATIONS

$I_s = 10^{-15} A = 1 fA$
 forward biased $V_o > 0$
 $I_d(0.6V) = (10^{-15} A)(10^{0.6/60mV}) = 10^{-5} A$
 $I_d(0.66V) = 10^{-4} A = 0.1 mA$
 $I_d(0.72V) = 1 mA$
 $I_d(0.626V) = 27 \mu A$
 $e^x = 10^{x/ln 10}$




→ current if $V_o > \sim 0.7V$
 if diode on: —●—
 if diode off: —○—

$$I_o(V_o) = I_s (e^{V_o/V_{th}} - 1)$$

$$\approx \begin{cases} -I_s & V_o < 100 mV \\ 0 & V_o = 0 \\ I_s e^{V_o/V_{th}} & V_o > 100 mV \end{cases}$$

⇒ $I_o = I_s 10^{V_o/60mV}$ at R.T

Phasor

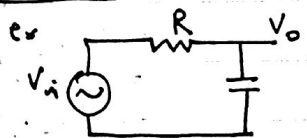

$$V_o = V_i - C \frac{dV_o}{dt} R$$

magnitude

$$\left| \frac{a + bj}{c + dj} \right| = \frac{\sqrt{a^2 + b^2}}{\sqrt{c^2 + d^2}}$$

$$\angle \frac{a + bj}{c + dj} = \angle a + bj - \angle c + dj$$

Complex *s

Rectangular form:

$$n = \alpha + jb$$

$$c = \sqrt{\alpha^2 + b^2}$$

$$\theta = \tan^{-1} \left(\frac{b}{a} \right)$$

polar form:

$$n = c e^{j\theta} = c \angle \theta^\circ$$

↑ phase mag

Steady state



$$V(t) = d \cos(\omega t + \theta)$$

$$\cos(\omega t + \theta) = -\sin \theta \sin(\omega t) + \cos \theta \cos(\omega t)$$

$$V_{in}(t) = d(\cos \theta \cos(\omega t) - \sin \theta \sin(\omega t))$$

$$= X \cos \omega t - Y \sin \omega t$$

$$V_{out}(t) = \beta \cos(\omega t + \theta_{out}) = U \cos(\omega t) - Z \sin(\omega t)$$

Zseries

$$\textcircled{1} Z_{series} = R + \frac{1}{j\omega C} = \frac{1 + j\omega RC}{j\omega C}$$

$$= \frac{1 + j\omega/\omega_p}{j\omega C} \leftarrow Z_{ZERO}$$

← pole

$$= \begin{cases} \frac{1}{j\omega C} & \omega \ll \omega_p \\ \frac{1 + j}{j\omega RC} & \omega = \omega_p \\ R & \omega \gg \omega_p \end{cases}$$

$$\textcircled{2} |Z_{series}| = \begin{cases} \frac{1}{\omega C} & \omega \ll \omega_p \\ \frac{1}{\sqrt{2}} \frac{1}{\omega C} & \omega = \omega_p \\ R & \omega \gg \omega_p \end{cases}$$

$$\textcircled{3} \angle Z_{series} = \begin{cases} -90 & \omega \ll \omega_p \\ -45 & \omega = \omega_p \\ 0 & \omega \gg \omega_p \end{cases} \leftarrow \frac{1 + j}{j}$$

$$Z_{parallel} = \frac{Z_R Z_C}{Z_R + Z_C} = \frac{R}{j\omega C R + 1} = \frac{R}{1 + j\omega RC}$$

$$= \frac{R}{1 + j\omega/\omega_p}$$

$$= \begin{cases} R & \omega \ll \omega_p \\ \frac{R}{\sqrt{2}} & \omega = \omega_p \\ \frac{1}{j\omega C} & \omega \gg \omega_p \end{cases}$$

$$\textcircled{1} Z_{parallel} = \begin{cases} R & \omega \ll \omega_p \\ \frac{R}{\sqrt{2}} & \omega = \omega_p \\ \frac{1}{j\omega C} & \omega \gg \omega_p \end{cases}$$

$$\textcircled{2} \angle Z_p = \begin{cases} 0 & \omega \ll \omega_p \\ -45 & \omega = \omega_p \\ -90 & \omega \gg \omega_p \end{cases}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega/\omega_p)^2}}$$

$$\angle H(j\omega) = -\tan^{-1}(\omega/\omega_p)$$

Root Mean Square

$$\begin{cases} V_{RMS} = \frac{V_{op}}{\sqrt{2}} \\ V_{op} = 2V_{avg} \\ V_{op} = \sqrt{2} \cdot V_{RMS} \end{cases}$$

$$P_{avg} = \frac{1}{T} \int_0^T p(t) dt = \frac{V_{op}^2}{2R}$$

$$V_{avg} = \frac{1}{T} \int_0^T \sin(\omega t) dt = 0$$

tan approx

$$\begin{cases} \tan(\pm 45) = \pm 1 \\ \tan(0) = 0 \\ \tan^{-1}(x) = x \quad (x < 1) \\ \tan^{-1}(x) = \frac{\pi}{2} \quad (x \gg 1) \end{cases}$$

$\frac{V_o}{V_i}$	$\frac{P_o}{P_{in}}$	dB
1	1	0
10	10^2	20
$\frac{1}{10}$	10^{-2}	-20
2	4	6
$\sqrt{2}$	2	3
$\frac{1}{\sqrt{2}}$	$\frac{1}{2}$	-3

$\frac{P_o}{P_i} = 10 \cdot \log_{10} \left(\left(\frac{V_o}{V_i} \right)^2 \right) = 20 \log_{10} \left(\frac{V_o}{V_i} \right)$


$r[\text{dB}] = 10r[\text{B}] = 10 \log_{10} \left(\frac{P}{P_{ref}} \right)$

① $1 \text{ dB} = 10 \log_{10} \left(\frac{P}{P_{ref}} \right)$

② $10 \log_{10} (2) = 3 \text{ dB} \rightarrow 10^{\frac{3}{10}} = 2$

③ $\sqrt{10} \approx 3.15 \rightarrow 10^{\frac{1}{2}} = 3.15 \rightarrow 2 \text{ dB}$

④ $2 \text{ dB} = 10 \log_{10} (1.6)$

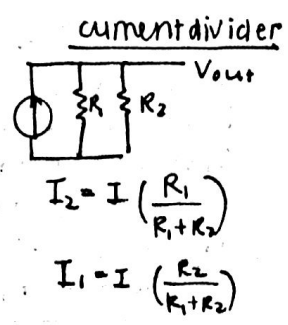

INDUCTOR

$V_L = L \frac{di}{dt}$

$W = \frac{1}{2} L i^2$

$P = IV = L \frac{di}{dt} i$

DATE: _____

capacitors

$V = E \cdot l$

$Q = C_{eq} V_{total}$

$I_c = C \cdot \frac{dV_c}{dt}$

$V_c(t) = V[t_0] + \int_{t_0}^t I_c dt$

$W = \frac{1}{2} C V^2$

$P = IV = C \cdot \frac{dV}{dt} \cdot V$

$I(t) - I_0 = m(t - t_0)$

$V_{in}(t) = |V_i| \cos(\omega t + \theta)$

$V_{out}(t) = |H(j\omega)| |V_{in}| \cos(\omega t + \theta_i + \angle H(j\omega))$

quality factor

$Q = \frac{\text{Energy Stored}}{\text{Energy dissipated/cycle}}$

$= \frac{\text{Energy stored}}{\frac{\text{Energy dissipated}}{\text{sec}} \cdot \frac{1}{\omega_0} \left[\frac{\text{cycles}}{\text{sec}} \right]}$

$= W \cdot \frac{L}{K}$


transients

① $V(0) < V_{\infty}$


$V_{out} = V_{\infty} + [V(0) - V_{\infty}] e^{-t/\tau}$

$\tau = RC$

$\approx e^{-1} = 0.37$

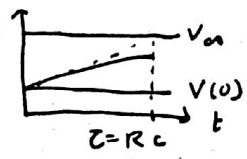

② $V(0) > V_{\infty}$

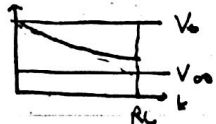

$V_{out} = V_{\infty} + [V(0) - V_{\infty}] e^{-t/\tau}$

$= V_{\infty} + [V(0) - V_{\infty}] (1 - t/\tau)$

$= [V(0) - V_{\infty}] (-t/\tau) + V_{\infty}$

Slope = $-\frac{[V(0) - V_{\infty}]}{RC}$


$\frac{V}{V_0}$	$\frac{P}{P_0}$	dB
1	1	0
10	10^2	20
10^2	10^4	40
10^{-1}	10^{-2}	-20
10^{-2}	10^{-4}	-40
2	4	6
4	16	12
8	64	18

20 dB decade

-20 dB decade

6 dB octave

octave

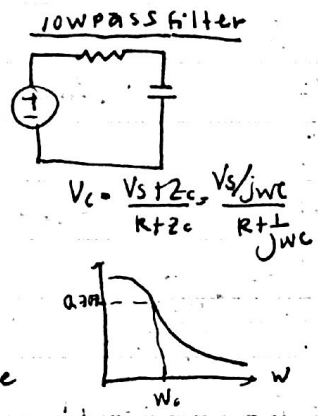


Digital circuit

Freq = $f = \frac{1}{T}$

$V(nT) = 0 \Leftrightarrow X_n = 0$

$V(nT) = V_{dd} \Leftrightarrow X_n = 1$

within 20% accuracy

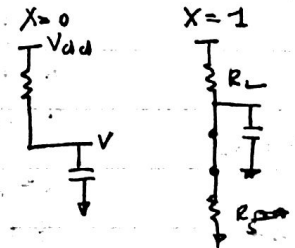

- ① n bits $\Rightarrow 2^n$ states (0, 1)
- ② n states $\Rightarrow \log_2 n$ bits
- ③ $\omega_p = 2\pi f = \frac{1}{RC}$
- $f_x < \frac{f_s}{2}$, $f_x \approx \frac{f_s}{2}$, $T_x = 2T_s$, $T_x = 2T_s$


LC TANK in parallel & series

① $Z_p = \frac{Z_L Z_C}{Z_L + Z_C} = \frac{j\omega L}{j\omega C} \cdot \frac{1}{(j\omega C + j\omega L)} = \frac{j\omega L}{1 - \omega^2 LC}$

② $Z_o = R + j\omega L + \frac{1}{j\omega C} = R + \frac{1 - \omega^2 LC}{j\omega C}$

③ $Q = \frac{\omega_p L}{R} = (\omega_p C R)^{-1} = \frac{1}{\omega_p C R}$

$\omega_p = \frac{1}{\sqrt{LC}}$

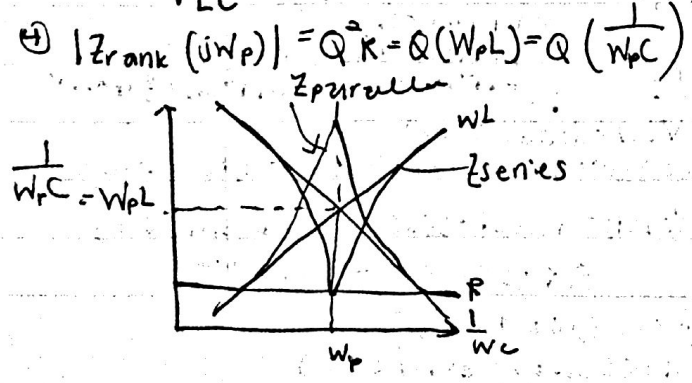

* conductivity $\sigma = \frac{1}{\rho}$

$\frac{\rho L}{A} = R$

$f_x < \frac{f_s}{2}$

$T_x = 2T_s$

* Sampling

$v(t) = \cos(2\pi(f_s + f)nt)$

$= \sin \left[2\pi n + 2\pi \frac{f}{f_s} n \right]$