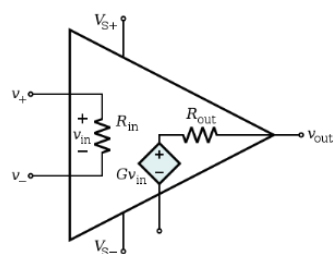



delta-wye



wheatstone resonance

$$V_{out} \approx \frac{V_0}{4} \left( \frac{\Delta R}{R} \right)$$
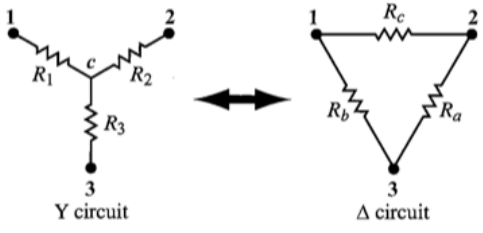
$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (\text{RLC circuit}).$$




$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} \quad R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

equivalence

| To Determine | Method                                   | Can Circuit Contain Dependent Sources? | Relationship               |
|--------------|--|--|----------------------------|
| $v_{Th}$     | Open-circuit $v$                         | Yes                                    | $v_{Th} = v_{oc}$          |
| $v_{Th}$     | Short-circuit $i$ (if $R_{Th}$ is known) | Yes                                    | $v_{Th} = R_{Th} i_{sc}$   |
| $R_{Th}$     | Open/short                               | Yes                                    | $R_{Th} = v_{oc} / i_{sc}$ |
| $R_{Th}$     | Equivalent $R$                           | No                                     | $R_{Th} = R_{eq}$          |
| $R_{Th}$     | External source                          | Yes                                    | $R_{Th} = v_{ex} / i_{ex}$ |

$i_N = v_{Th} / R_{Th}; R_N = R_{Th}$

filters

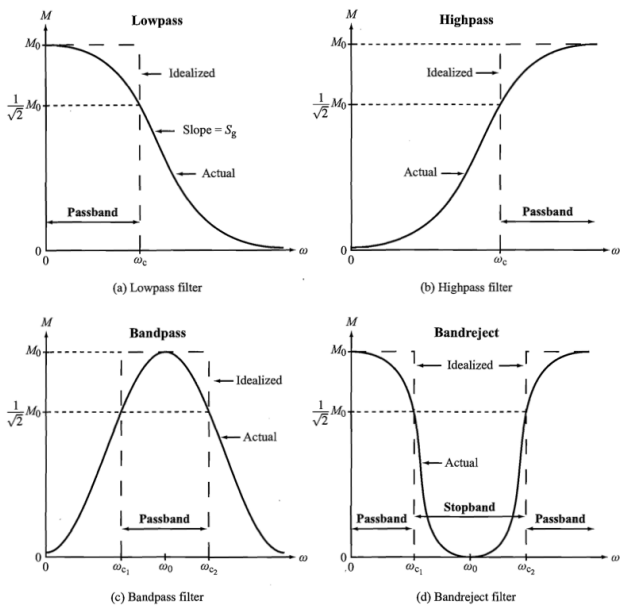


second order

| Series RLC   | Parallel RLC   |
|--|--|
| <b>Input:</b> dc circuit with switch action @ $t = 0$<br>  | <b>Input:</b> dc circuit with switch action @ $t = 0$<br>  |
| <b>Total Response</b>  | <b>Total Response</b>  |
| <b>Overdamped</b> ( $\alpha > \omega_0$ )<br>$v_C(t) = v_C(\infty) + A_1 e^{s_1 t} + A_2 e^{s_2 t}$<br>$A_1 = \frac{\frac{1}{C} i_C(0) - s_2 [v_C(0) - v_C(\infty)]}{s_1 - s_2}$<br>$A_2 = \frac{[\frac{1}{C} i_C(0) - s_1 [v_C(0) - v_C(\infty)]}{s_2 - s_1}$ | <b>Overdamped</b> ( $\alpha > \omega_0$ )<br>$i_L(t) = i_L(\infty) + A_1 e^{s_1 t} + A_2 e^{s_2 t}$<br>$A_1 = \frac{\frac{1}{L} v_L(0) - s_2 [i_L(0) - i_L(\infty)]}{s_1 - s_2}$<br>$A_2 = \frac{[\frac{1}{L} v_L(0) - s_1 [i_L(0) - i_L(\infty)]}{s_2 - s_1}$ |
| <b>Critically Damped</b> ( $\alpha = \omega_0$ )<br>$v_C(t) = v_C(\infty) + (B_1 + B_2 t) e^{-\alpha t}$<br>$B_1 = v_C(0) - v_C(\infty)$<br>$B_2 = \frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]$   | <b>Critically Damped</b> ( $\alpha = \omega_0$ )<br>$i_L(t) = i_L(\infty) + (B_1 + B_2 t) e^{-\alpha t}$<br>$B_1 = i_L(0) - i_L(\infty)$<br>$B_2 = \frac{1}{L} v_L(0) + \alpha [i_L(0) - i_L(\infty)]$   |
| <b>Underdamped</b> ( $\alpha < \omega_0$ )<br>$v_C(t) = v_C(\infty) + e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t)$<br>$D_1 = v_C(0) - v_C(\infty)$<br>$D_2 = \frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)] / \omega_d$                      | <b>Underdamped</b> ( $\alpha < \omega_0$ )<br>$i_L(t) = i_L(\infty) + e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t)$<br>$D_1 = i_L(0) - i_L(\infty)$<br>$D_2 = \frac{1}{L} v_L(0) + \alpha [i_L(0) - i_L(\infty)] / \omega_d$                      |
| <b>Auxiliary Relations</b>   |  |
| $\alpha = \begin{cases} \frac{R}{2L} & \text{Series RLC} \\ \frac{1}{2RC} & \text{Parallel RLC} \end{cases}$   | $\omega_0 = \frac{1}{\sqrt{LC}}$<br>$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$<br>$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$<br>$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$  |

RLC & vars

| Property                        | R                                    | L                                     | C                                     |
|---------------------------------|--------------------------------------|---------------------------------------|---------------------------------------|
| $i-v$ relation                  | $i = \frac{v}{R}$                    | $i = \frac{1}{L} \int v dt' + i(t_0)$ | $i = C \frac{dv}{dt}$                 |
| $v-i$ relation                  | $v = iR$                             | $v = L \frac{di}{dt}$                 | $v = \frac{1}{C} \int i dt' + v(t_0)$ |
| $p$ (power transfer in)         | $p = i^2 R$                          | $p = Li \frac{di}{dt}$                | $p = Cv \frac{dv}{dt}$                |
| $w$ (stored energy)             | 0                                    | $w = \frac{1}{2} Li^2$                | $w = \frac{1}{2} Cv^2$                |
| Series combination              | $R_{eq} = R_1 + R_2$                 | $L_{eq} = L_1 + L_2$                  | $C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$  |
| Parallel combination            | $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$ | $L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$  | $C_{eq} = C_1 + C_2$                  |
| dc behavior                     | no change                            | short circuit                         | open circuit                          |
| Can $v$ change instantaneously? | yes                                  | yes                                   | no                                    |
| Can $i$ change instantaneously? | yes                                  | no                                    | yes                                   |

op amp circuits

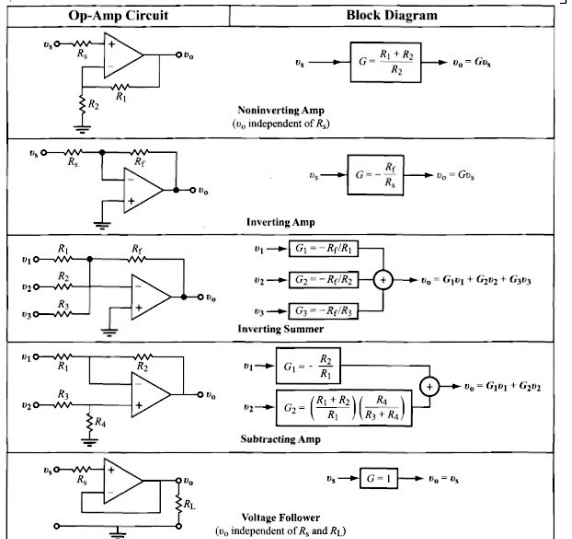

RLC transient responses

| Circuit              | Diagram   | Response  |
|----------------------|---|---|
| RC                   | <b>Input:</b> dc circuit with switch action @ $t = T_0$<br> | $v(t) = v(\infty) + [v(T_0) - v(\infty)]e^{-(t-T_0)/\tau}$<br>$(\tau = RC) \quad (\text{for } t \geq T_0)$  |
| RL                   | <b>Input:</b> dc circuit with switch action @ $t = T_0$<br> | $i(t) = i(\infty) + [i(T_0) - i(\infty)]e^{-(t-T_0)/\tau}$<br>$(\tau = L/R) \quad (\text{for } t \geq T_0)$ |
| Ideal integrator     |   | $v_{out}(t) = -\frac{1}{RC} \int v_1 dt' + v_{out}(t_0)$  |
| Ideal differentiator |   | $v_{out}(t) = -RC \frac{dv_1}{dt}$  |